

ID:

Name:

**Brac University****Set: 1**

Semester: Fall 2022

Course No: CSE250

Course Title: CIRCUITS AND ELECTRONICS

Date: November 11, 2022

Midterm Exam

Full marks: 50 (+5 Bonus)


Duration: 1 hour 15 minutes

**All the questions are mandatory.** Numbers inside box brackets indicate marks.


### Question 1 of 3 [20 marks] [CO1, CO2, CO4]

**Part A:** The plot below shows the current response of a resistor when different voltages are applied across it. **Determine** the value of the resistor from the plot. Show calculation.

[2]

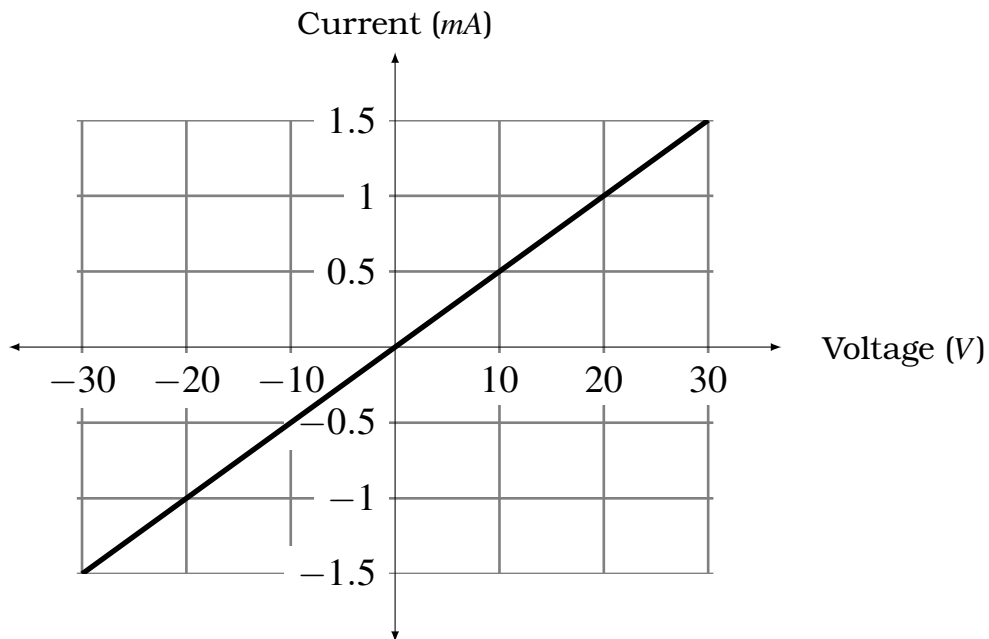

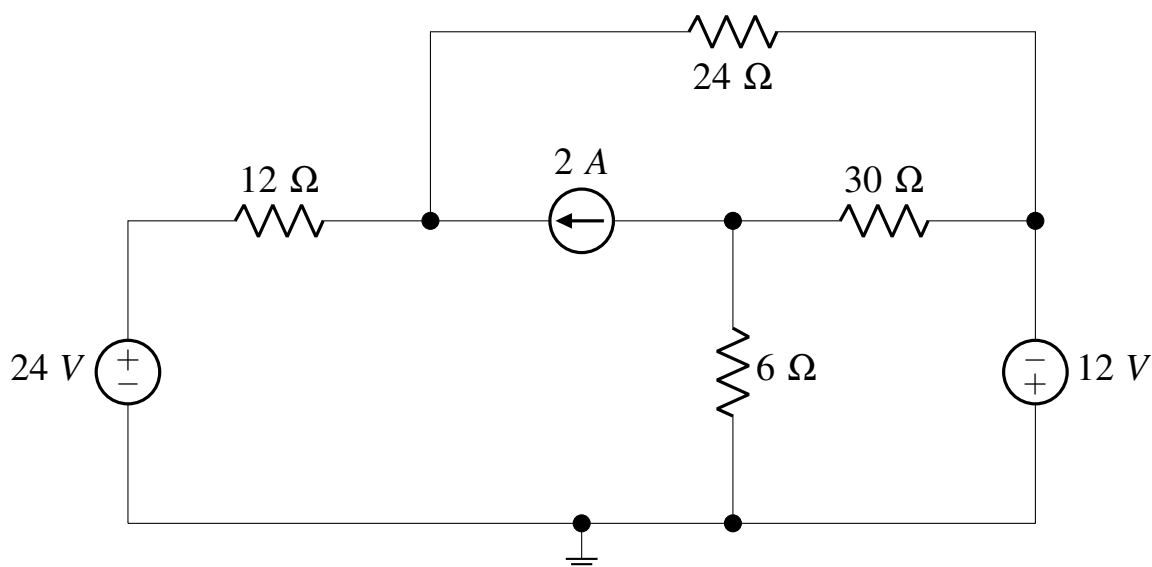
**Part B:** Consider the circuit shown below.



- (i) **Apply Nodal/Mesh Analysis** to **identify** the values of the node voltages/mesh currents. *(Equations must be highlighted using boxes).* [14]
- (ii) **Determine** the power supplied/absorbed by the current source (with appropriate  $\pm$  sign). [4]

## Question 2 of 3 [20 marks] [CO2, CO4]

Consider the circuit shown below.

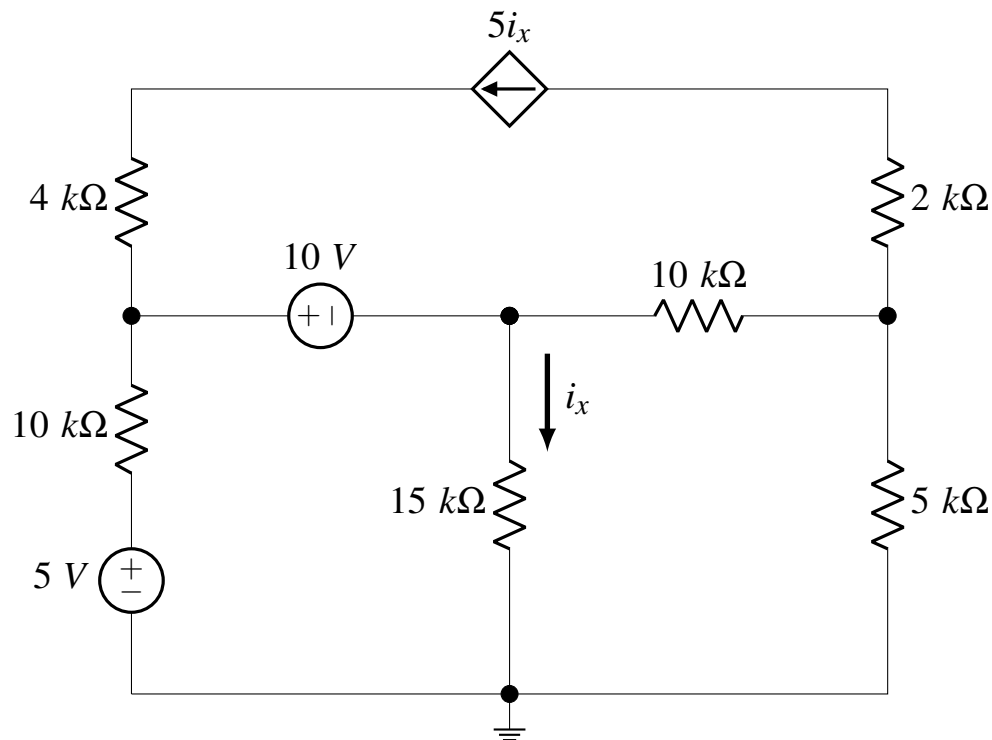

- (i) **Apply Nodal/Mesh Analysis** to **identify** the values of the node voltages/mesh currents. *(Equations must be highlighted using boxes).* [16]
- (ii) **Determine**  $i_x$  and the current through the 10 V voltage source. [2+2]

## Question 3 of 3 [15 marks] [CO2, CO3, CO4]

**Part A:** The two equations below are derived by applying KVL to a linear circuit. [3]

$$-12 + 2I_2 + 4(I_2 - I_1) = 0 \quad \dots\dots\dots(i),$$

$$4(I_2 - I_1) + 8 + 6I_1 = 0 \quad \dots\dots\dots(ii),$$

where  $I_1$  and  $I_2$  are the loop currents, in ampere units. **Draw** the circuit and label the component values appropriately.

**Part B:** Use **Source Transformation** to **analyze** the circuit shown below. **Determine**  $V_0$ . [12]

