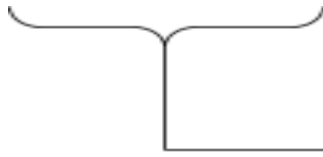


Student ID:	22301078	Lab Section:	30
Name:	Sumaiya Hossain Surovi	Question Set:	E

Simulation Labtest CSE250 Fall'23

Make copy of this doc > Edit with your answers > Download as PDF > Submit




File > Make a copy > Rename > Make a copy

Answers

A. Phase difference between the indicated voltage and current

Quantity	Value
θ	0.046 degree

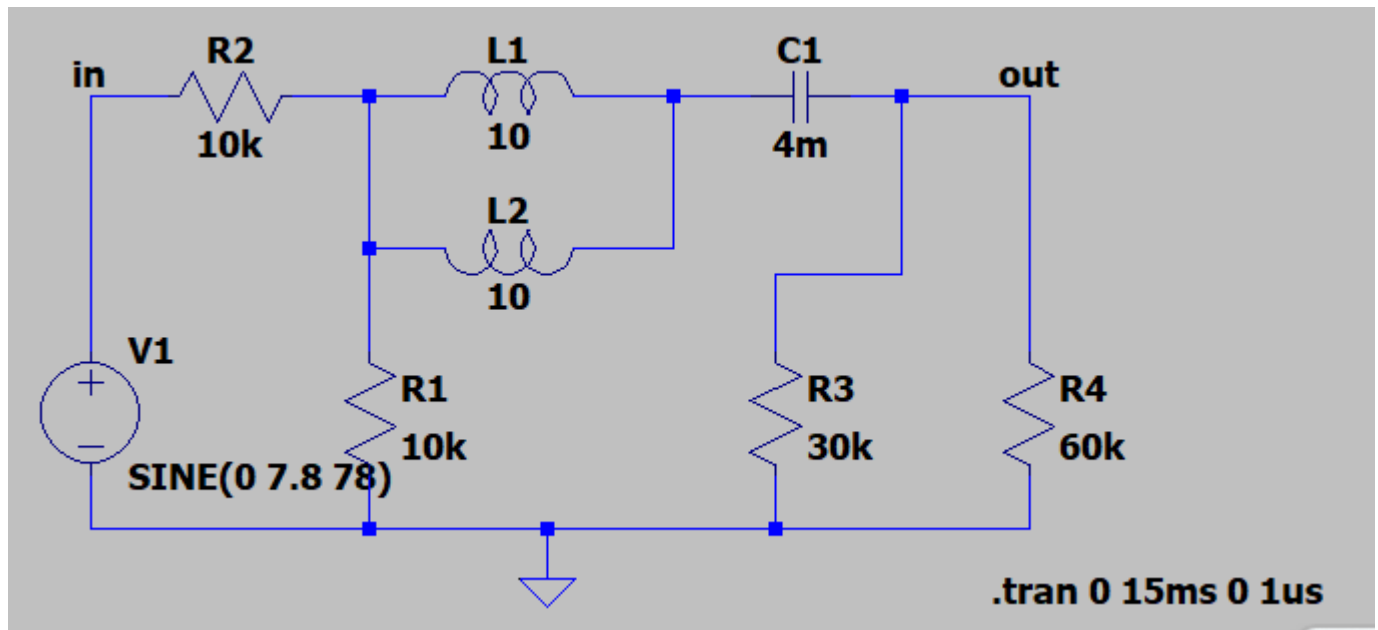B. Screenshot of schematic diagram from LTspice (simulation command must be visible)



C. Screenshot of the plot of the capacitor voltage and current as a function of time from LTspice

