

ID:

Name:

Set: 2

Brac University

Semester: Summer 2022

Course No: CSE250

Course Title: CIRCUITS AND ELECTRONICS


Date: September 09, 2022

Final Exam


Full marks: 50 (+5 Bonus)

Duration: 2 hours

## Question 1 of 3 [20 marks]

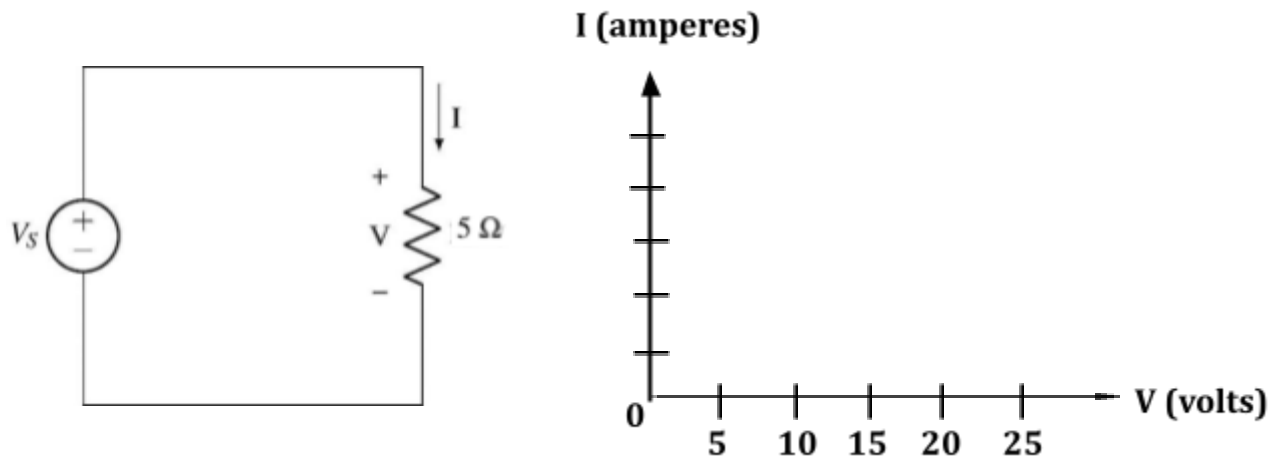

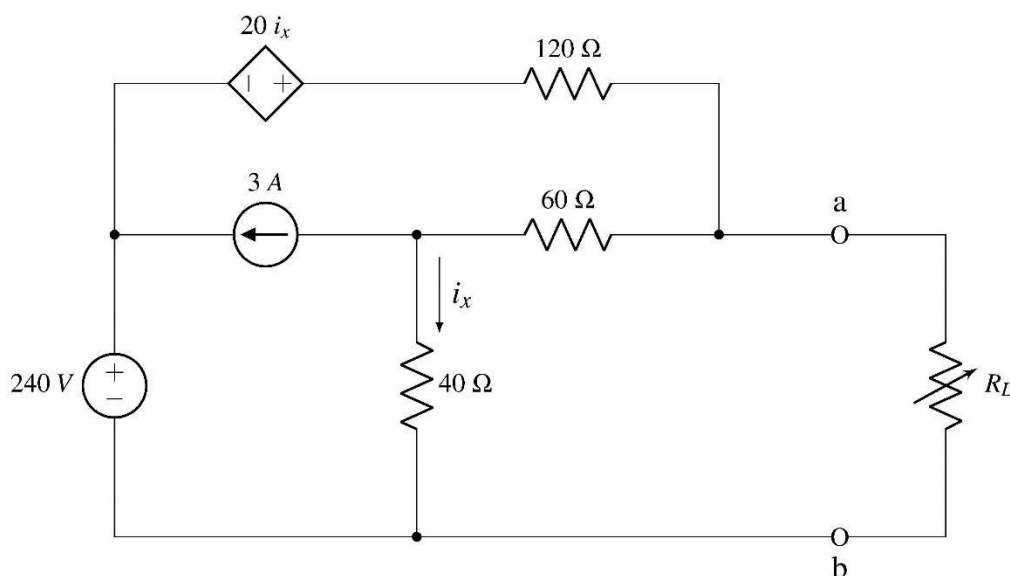
- **Draw the I-V characteristics** of the  $5\ \Omega$  resistor shown in the circuit above. Please redraw the plot template given above on your script. You must label the axes with appropriate values.  
(2 marks) [CO1]



- **Determine** the value of  $R_L$  that will draw **Maximum Power** from the rest of the circuit.  
(10 marks) [CO3, CO4]
- **Determine** that value of the **Maximum Power**.  
(8 marks) [CO2, CO4]


Set: 2

**Question 2 of 3 [20 marks]**

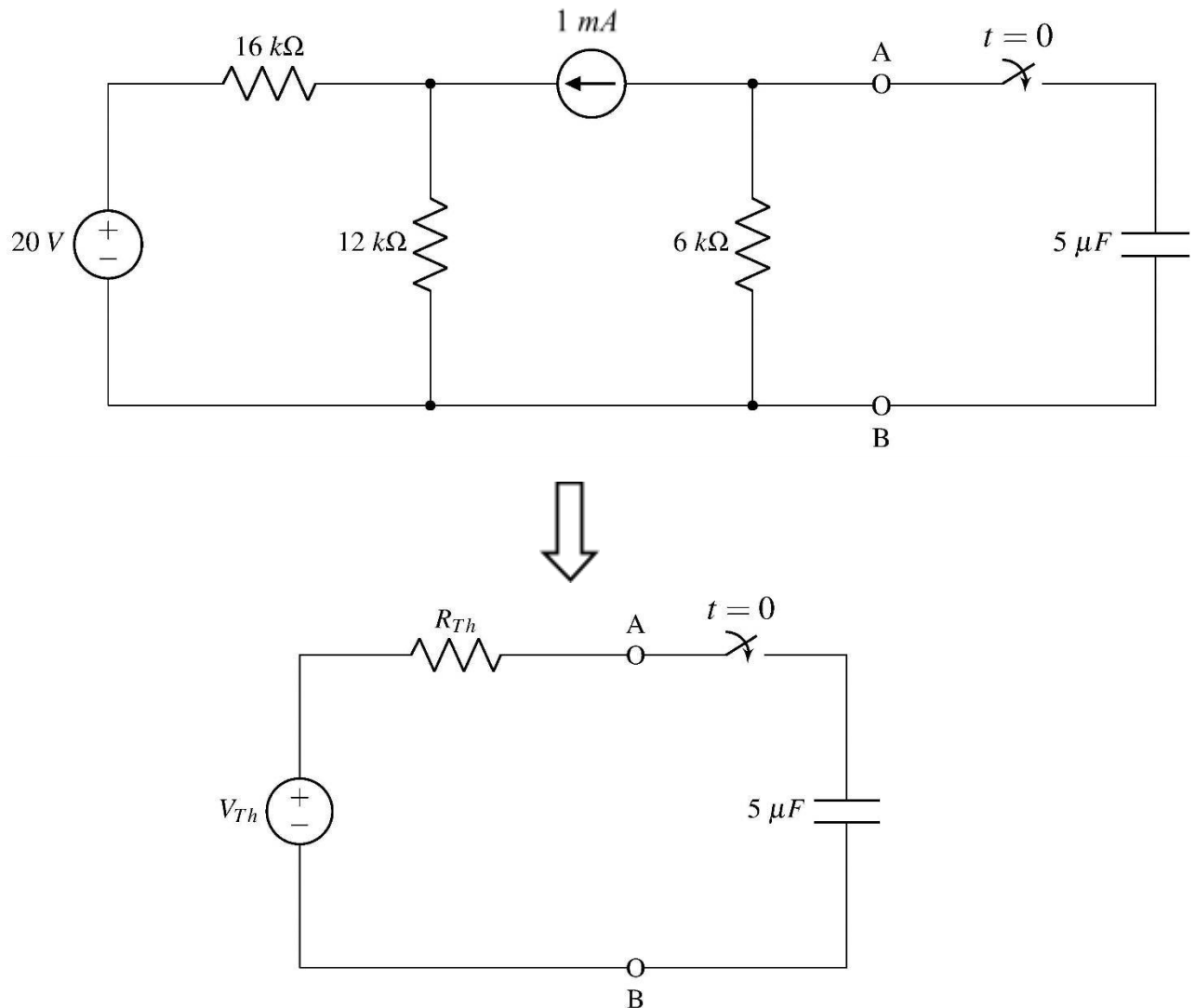


- **Reduce** the first circuit so that it takes the form of the 2nd circuit as shown above. [Hint: Use Thevenin's principle]  
(8 marks) [CO4]
- **Perform** transient analysis to determine  $v(0)$ ,  $v(\infty)$ , and  $v(t)$  for  $t > 0$ . Also, determine the **current through the capacitor** at  $t = 0.5 \text{ ms}$ .  
(9 marks) [CO5]

Set: 2

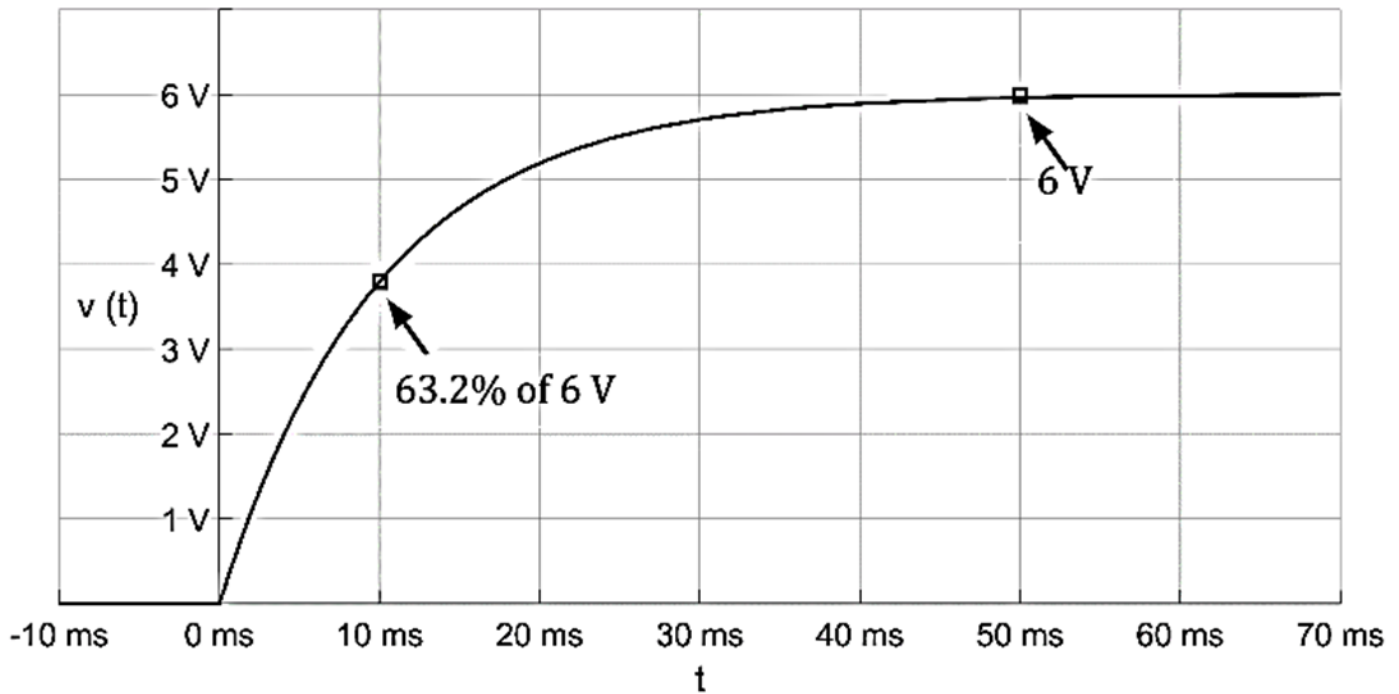

- The figure above shows the voltage response of a series RC circuit to a sudden DC voltage applied through an equivalent resistance of  $2\text{ k}\Omega$ . **Determine** the approximate **time constant** from the figure. Also, **determine** the value of the **capacitor** used in the RC circuit and find the **expression** for  $v(t)$  as only a function of  $t$ . [Hint: Time constant is the time required for the capacitor voltage to reach to 63.2% of its final value from an initially discharged state]  
(3 marks) [CO5]

**Question 3 of 3 [15 marks]**

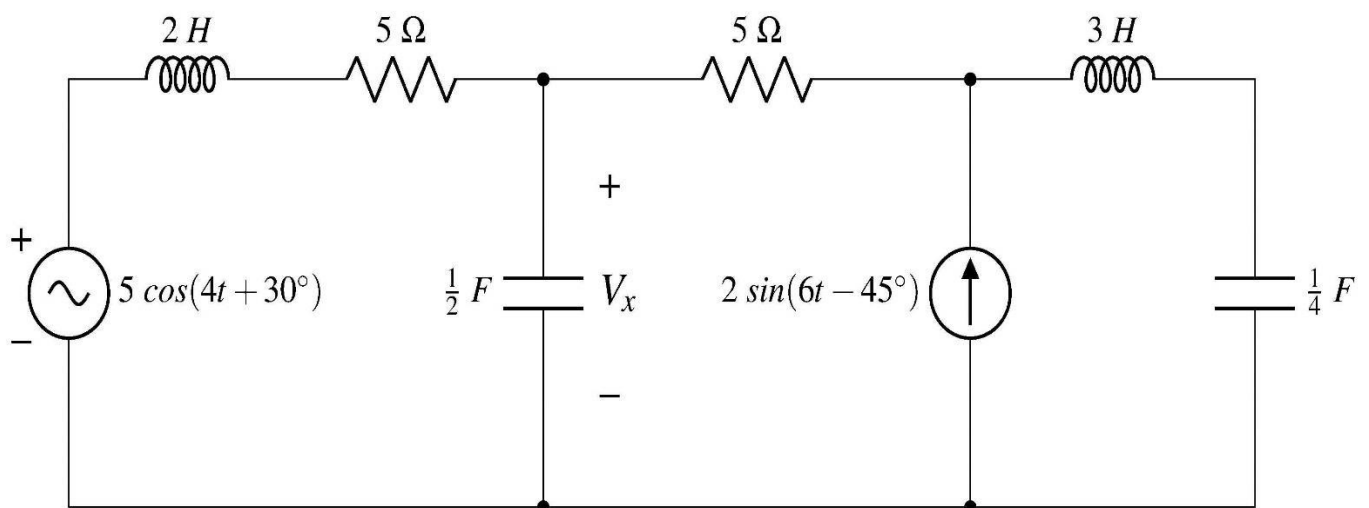

- Determine** the voltage  $v_x$ . [Hint: Use Superposition principle]  
(15 marks) [CO4, CO6]