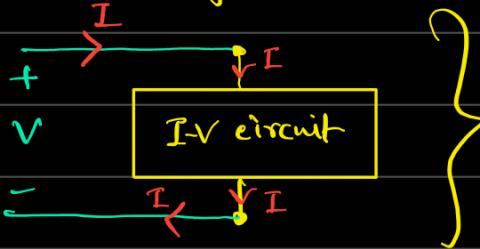


How to Guide: I-V Characteristics

- Shadman Shahriar (SDS)



- ① Please read through all the details.
- ② Both methods are useful. If asked for a graph first method is a bit easier. If asked for equation better use Method 2.
- ③ Both methods are actually same thing. If you are having trouble working with x volt and y current, use IV or IA to get a sense of how you should solve it.
- ④ You may use any circuit solving techniques such as: KCL, KVL, Nodal/Mesh Analysis, Source transformation, superposition etc.
- ⑤ Keep Passive Sign Convention in mind. That is:


The diagram shows a rectangular box labeled "IV circuit". Above the box, there is a horizontal line with an arrow pointing right, labeled "I". Below the box, there is another horizontal line with an arrow pointing left, labeled "I". Above the top line, there is a green "+" sign above a red "V" sign. Below the bottom line, there is a green "-" sign below a red "V" sign. To the right of the box, a large curly brace groups the text "Current should always enter through the (+ve) terminal and leave via (-ve)." with the diagram.

Current should always enter through the (+ve) terminal and leave via (-ve).

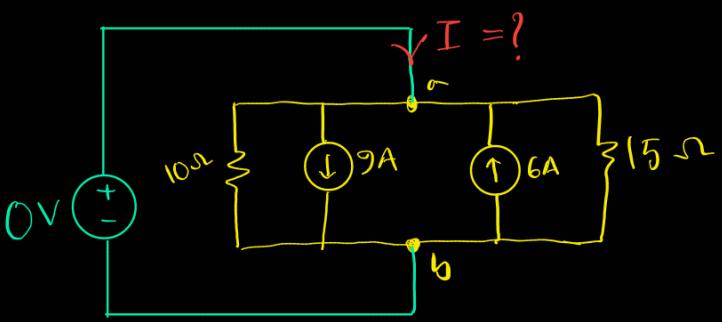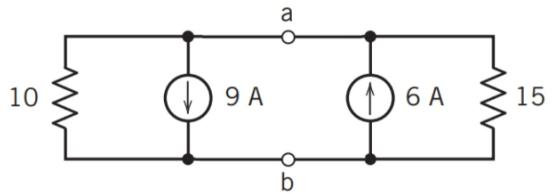Problem 1


- Derive the $I - V$ characteristics of the following circuit with respect to the terminals $a - b$.




$$V_a - V_b = 0V$$

$$\text{At } a: \frac{V_a - V_b}{10} = \frac{0}{10} A = 0A$$
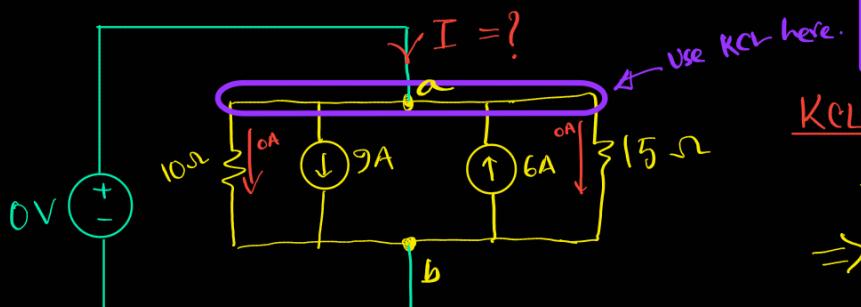
$$\text{At } b: \frac{V_a - V_b}{15} = \frac{0}{15} A = 0A$$



Similarly, for $1V$,

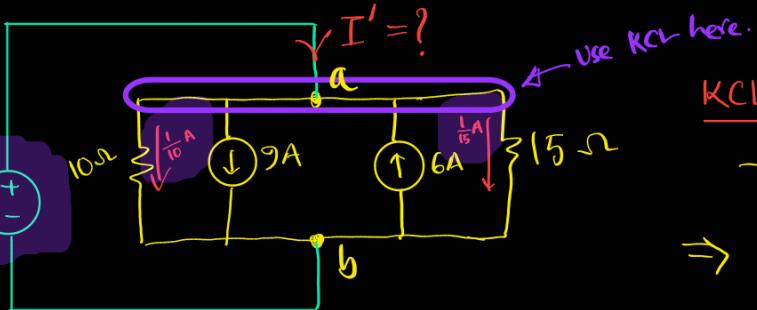


Method 1: Two data points

① Apply some voltage across the terminals using a $0V$ voltage source. (You can use any voltage you like.)


② Use $0A$ current source if voltage source can't be applied (e.g. another voltage src in parallel)

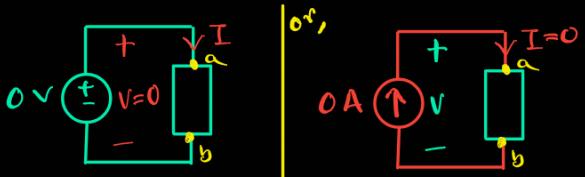③ Find current I supplied by the voltage source. (Notice the direction of current. Must follow passive sign convention for the circuit given in question)



④ Repeat for $1V$, find new current I' .

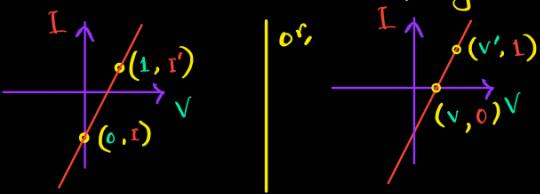⑤ Plot the two data points in graph and connect them via straight line.



⑥ Use $y = mx + c$ to get equation.

KCL @ Node a:

$$-I + 0 + 9 - 6 + 0 = 0$$

$$\Rightarrow I = 9 - 6$$

$$\therefore I = 3A$$

\therefore one data point $\Rightarrow (0, 3)$


KCL @ Node a:

$$-I' + \frac{1}{10} + 9 - 6 + \frac{1}{15} = 0$$

$$\Rightarrow I' = \frac{1}{10} + 9 - 6 + \frac{1}{15}$$



$$\therefore I' = 3.167 A$$

\therefore second data point $\Rightarrow (1, 3.167)$

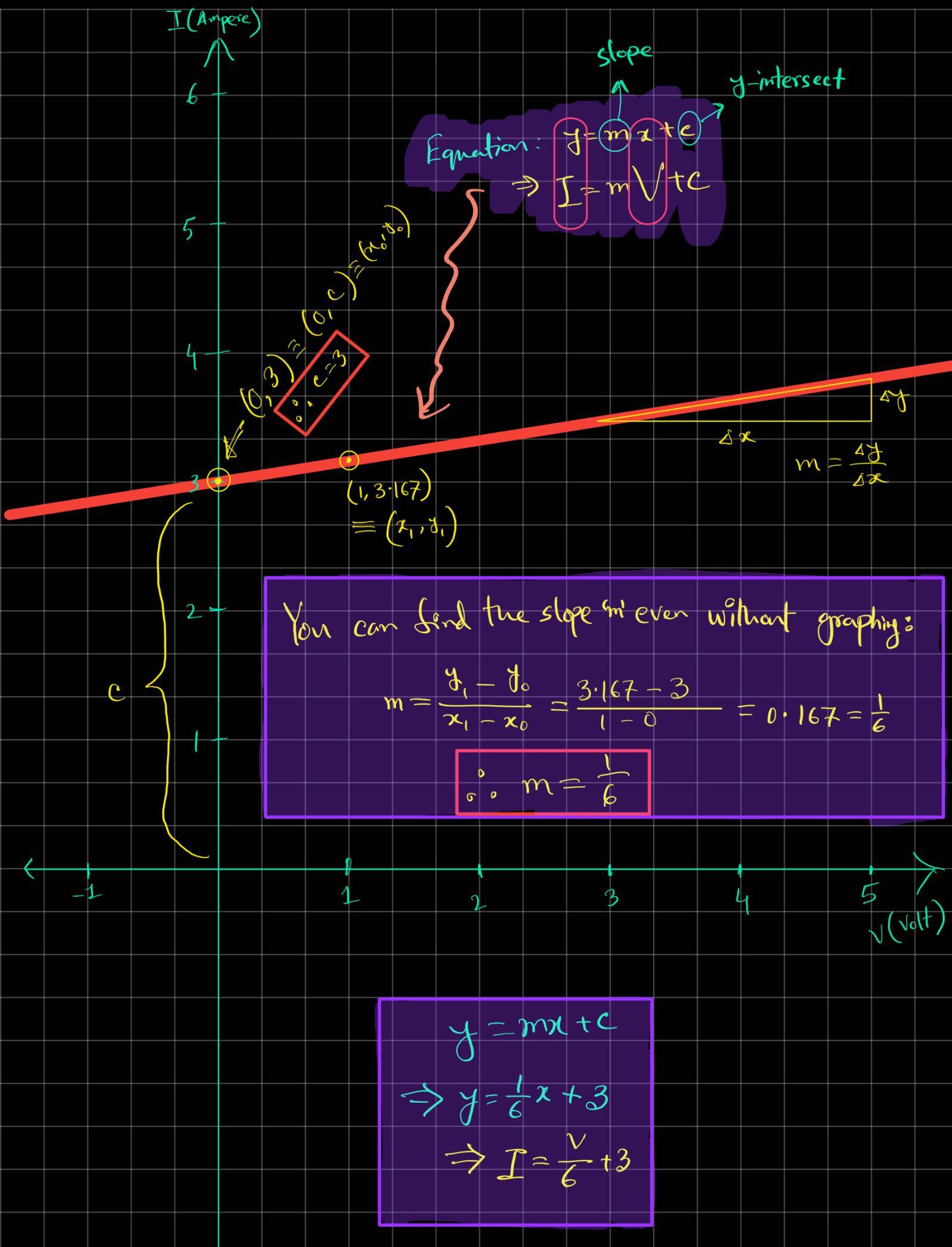

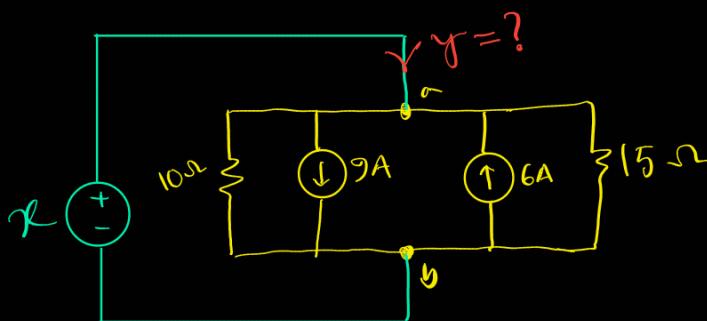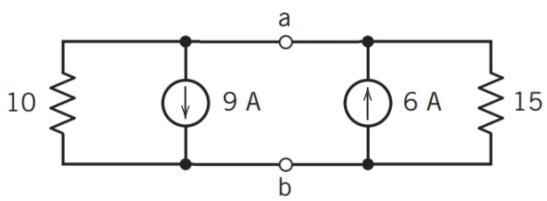Problem 1


- Derive the $I - V$ characteristics of the following circuit with respect to the terminals $a - b$.



$$V_a - V_b = x$$

$$10\Omega \quad \frac{V_a - V_b}{10} = \frac{x}{10} \text{ A}$$

$$15\Omega \quad \frac{V_a - V_b}{15} = \frac{x}{15} \text{ A}$$

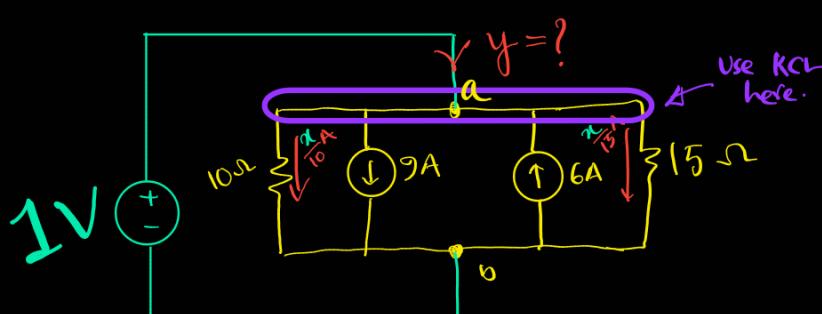


Method 2: x Volt - y current.

① Apply x voltage across the terminals using a voltage source of x volt. (This just like the 1V case as before, except you replace 1V with x everywhere)

⊗ Use current source if voltage source can't be applied (e.g. another voltage src in parallel)

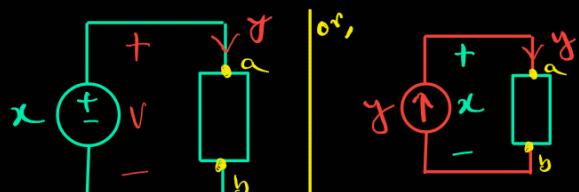② Find the current y supplied by the voltage source to the circuit.



③ Replace y with I and x with V for final answer.

KCL @ Node a:

$$-y + \frac{x}{10} + 9 - 6 + \frac{x}{15} = 0$$

$$\Rightarrow y = \frac{x}{10} + 9 - 6 + \frac{x}{15}$$

$$\Rightarrow y = x \left(\frac{1}{10} + \frac{1}{15} \right) + 3$$


$$\therefore y = \frac{x}{6} + 3$$

You directly get the equation !!


$$I = \frac{V}{6} + 3$$

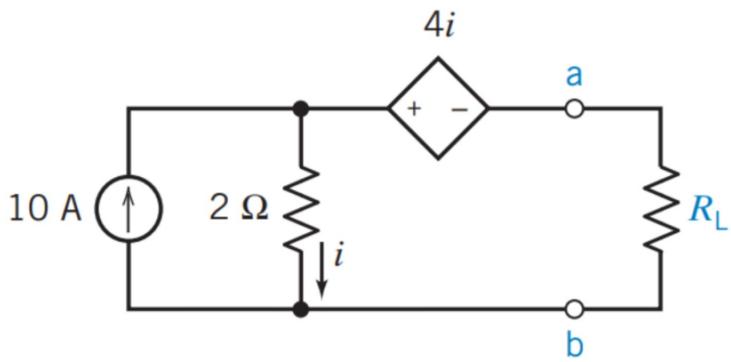Problem 2

- Derive the $I - V$ characteristics of the portion left to the terminals $a - b$.




$$\text{Ans: } I = -\frac{1}{2}V - 10$$

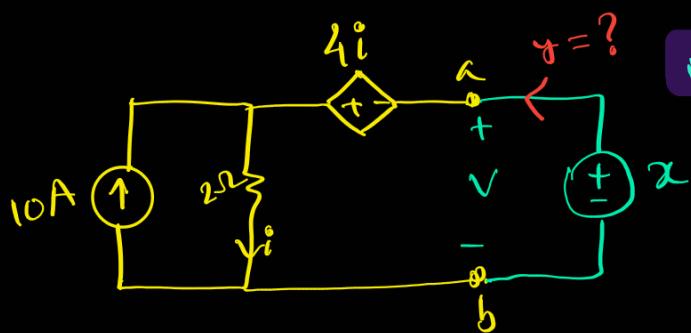

Notice the direction of current y follows positive sign convention for the I-V circuit.

Using Mesh analysis:

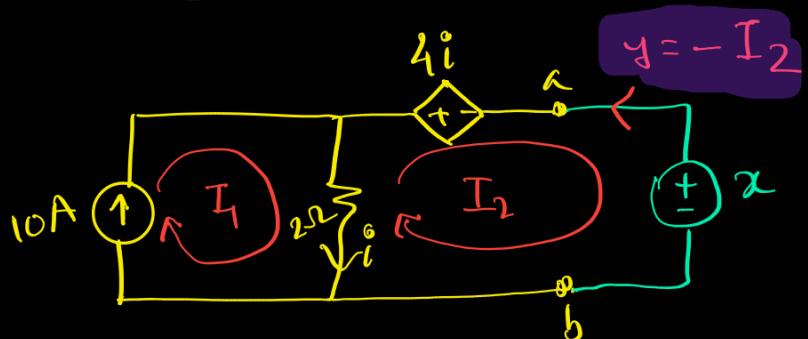

$$I_1 = 10$$

KVL @ 2:

$$I_2(2) - 2I_1 + 4i + x = 0$$

$$\Rightarrow 2I_2 - 2 \times 10 + 4(I_1 - I_2) + x = 0$$

$$\Rightarrow 2(-y) - 2 \times 10 + 4(10 - (-y)) + x = 0$$

Already a relation between x & y .


$$\Rightarrow -2y - 20 + 40 + 4y + x = 0$$

$$\Rightarrow x + 2y + 20 = 0$$

$$\Rightarrow y = -\frac{x}{2} - 10$$

$$I = -\frac{V}{2} - 10$$

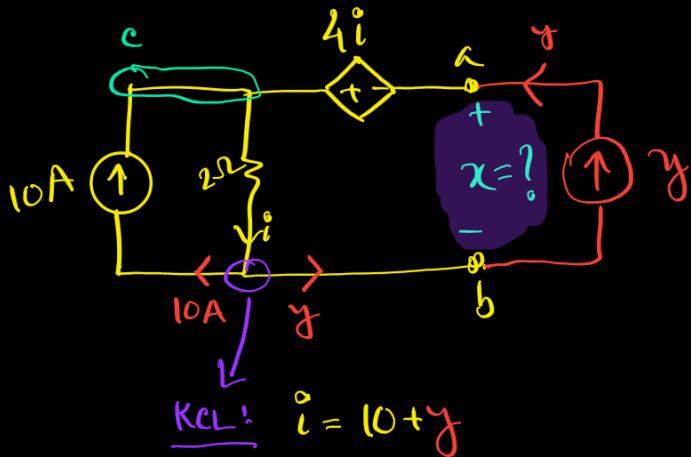There is actually an easier way to solve Problem 2. You don't even need Mesh Analysis. Read this first:



$$\begin{aligned}x &= V_a - V_b \\&= V_a - V_c + V_c - V_b \\&= -(V_c - V_a) + (V_c - V_b) \\&= -(4i) + 2 \times i \\&= -2i \\∴ x &= -2(10 + y)\end{aligned}$$

$$\Rightarrow -\frac{x}{2} = 10 + y$$


$$\therefore y = -\frac{x}{2} - 10$$

$$\boxed{\therefore I = -\frac{v}{2} - 10}$$

Rough


use 1A instead of y if you can't figure out what to do.

Here is the example:

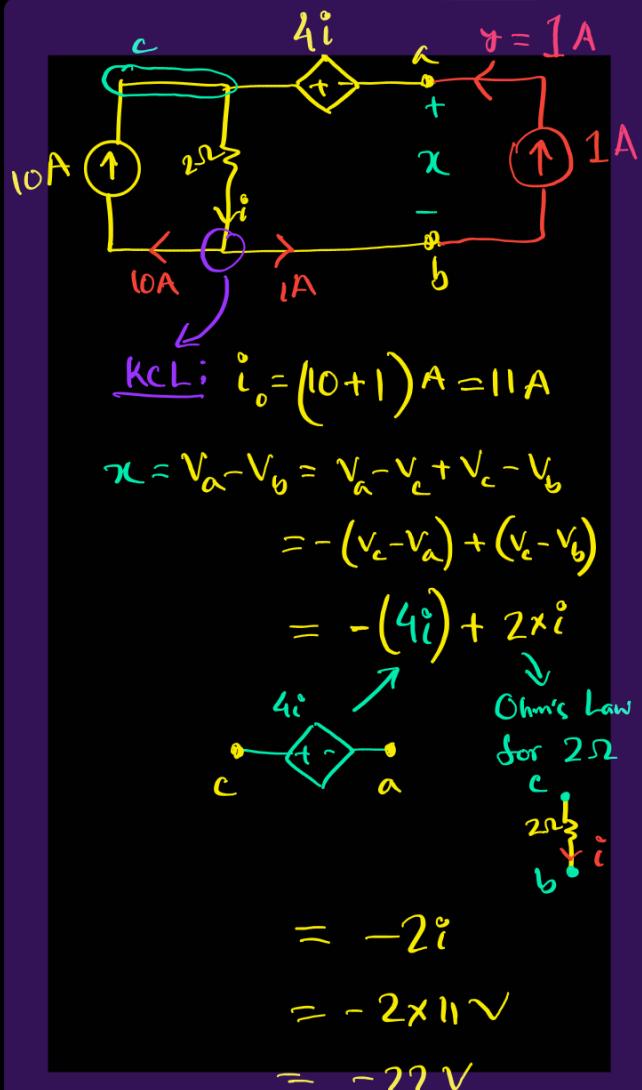

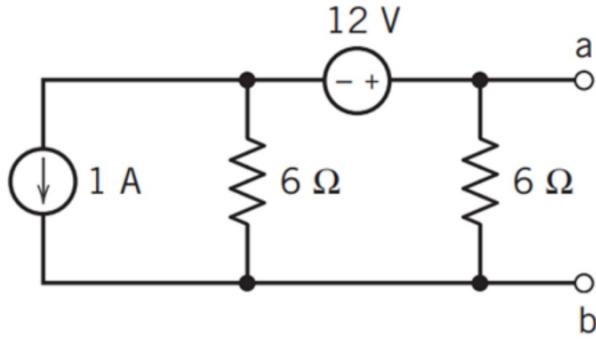Problem 3


- From the following circuit, derive the current-voltage characteristics equation between the terminals $a - b$.



$$\text{Ans: } I = \frac{1}{3}V - 1$$

Try to solve this yourself by applying IV first.

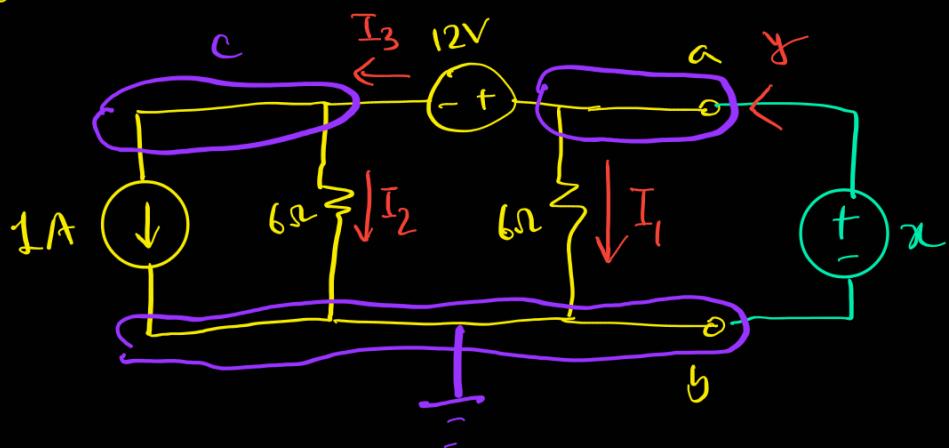Then replace IV with x . (I'm doing it with just x)
Do this for all problems discussed later as well.



$$V_a - V_b = x \Rightarrow V_a = x$$

$$V_a - V_c = 12 \Rightarrow x - V_c = 12 \Rightarrow V_c = x - 12$$

$$I_1 = \frac{V_a - V_b}{6} = \frac{x}{6}, \quad I_2 = \frac{V_c - V_b}{6} = \frac{(x-12) - 0}{6} = \frac{x}{6} - 2$$


KCL @ c: $I_3 = 1 + I_2$

KCL @ a: $y = I_1 + I_3 = I_1 + 1 + I_2 = \frac{x}{6} + 1 + \frac{x}{6} - 2$

$$\therefore y = \frac{x}{3} - 1 \Rightarrow I = \frac{y}{3} - 1$$

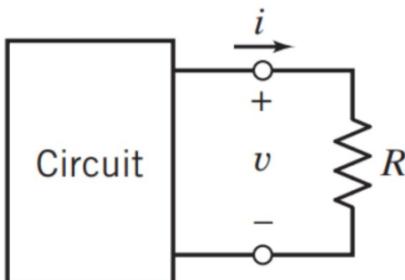
Problem 4

- A resistor, R , was connected to a circuit box as shown below. The current i was measured. The resistance was changed, and the current was measured again. The results are shown in the table.
 - Plot the relationship between i and v .
 - Draw a circuit diagram with minimum number of circuit elements that can give rise to the same $i - v$ curve derived in i.




R	i
2 k Ω	4 mA
4 k Ω	3 mA

Ans: $i = -\frac{1}{4}v + 6$

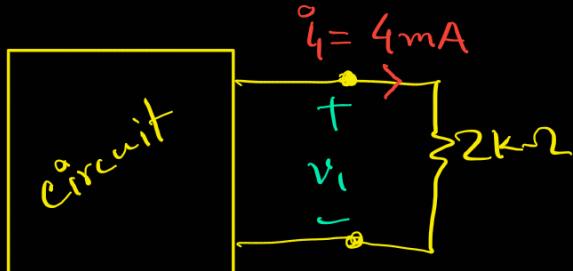

$$v_1 = 4 \text{ mA} \times 2 \text{ k}\Omega \\ = 8 \text{ V}$$

Data Point 1: (v_1, i_1)
 $= (8, 4)$

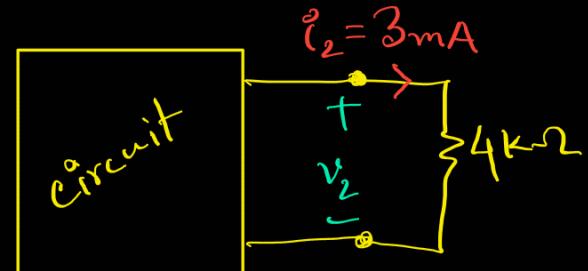


$$v_2 = 3 \text{ mA} \times 4 \text{ k}\Omega \\ = 12 \text{ V}$$

Data Point 2: (v_2, i_2)
 $= (12, 3)$

$$m = \frac{y_2 - y_1}{x_2 - x_1} = \frac{3 - 4}{12 - 8} = -\frac{1}{4}$$

④ But how do we find 'c' ?

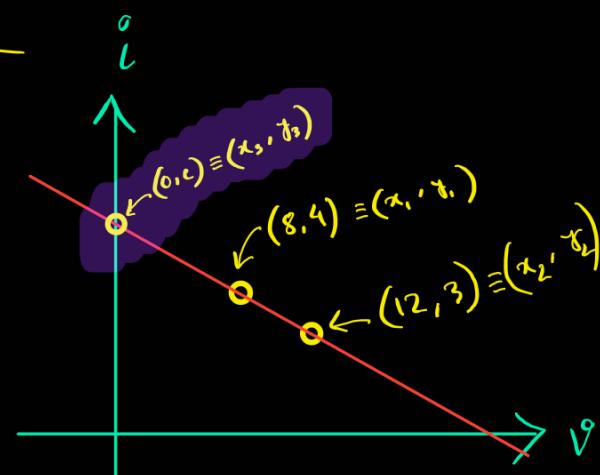Notice that (x_1, y_1) , (x_2, y_2) and $(0, c)$ are all points on the line.




Since (x_1, y_1) and $(x_3, y_3) \equiv (0, c)$ are on the same line, slope 'm' should be same as before $(-\frac{1}{4})$.

$$m = \frac{y_3 - y_1}{x_3 - x_1} = \frac{c - 4}{0 - 8} = \frac{c - 4}{-8}$$

$$\text{But, } m = \frac{-1}{4}. \quad \text{So, } \frac{c - 4}{-8} = \frac{-1}{4} \Rightarrow c = 4 + \frac{8}{4} = 6$$

$$\therefore y = mx + c \Rightarrow y = -\frac{1}{4}x + 6 \Rightarrow \boxed{i = -\frac{v}{4} + 6}$$




*) But how to find a proper circuit?

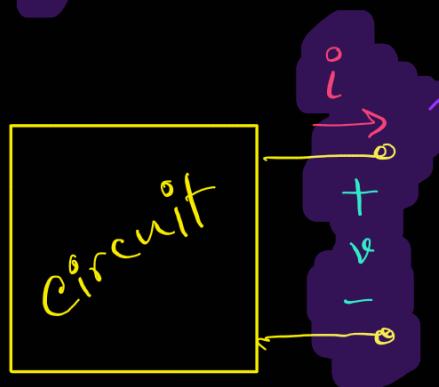


= ?

Notice how v and i are not following passive sign convention. This will be important.

We need to memorize a few I-V circuits:

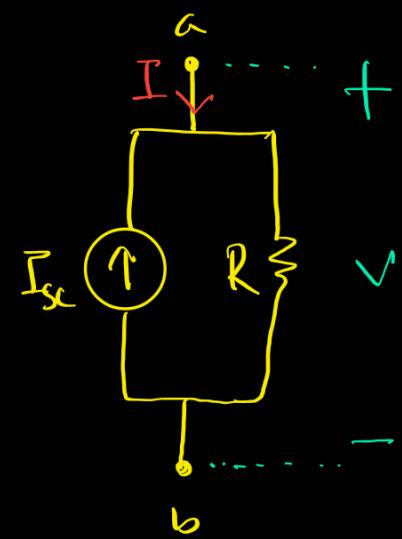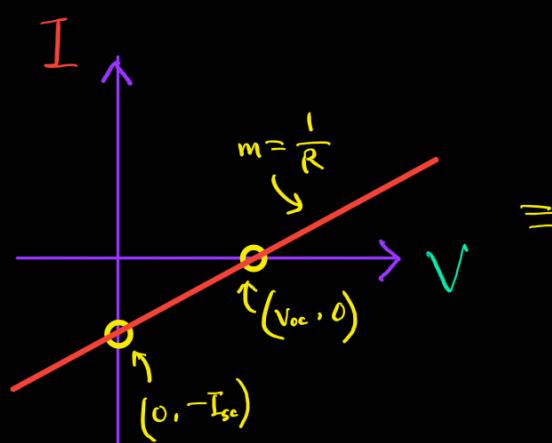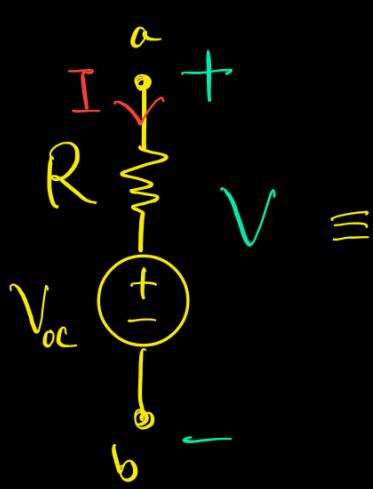

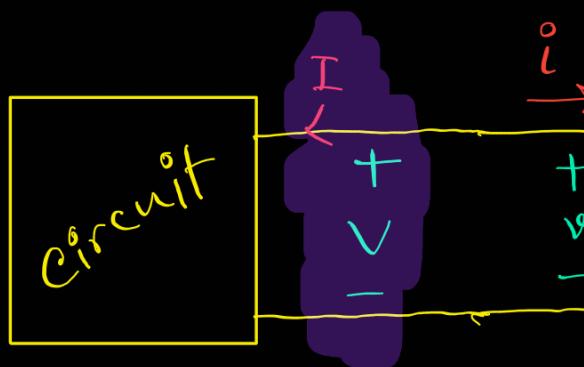Now, Since our given circuit doesn't follow Passive Sign convention, Let's fix it. I am denoting the proper direction with capital letters.



↑ follows passive sign convention.

$$V = v, \quad I = -i$$

We know from part (i) of the question,

$$i = -\frac{v}{4} + 6 \Rightarrow -I = \frac{-V}{4} + 6$$

$$\Rightarrow I = \frac{V}{4} - 6$$



Now the slope is positive as expected.

$$\therefore m = \frac{1}{4} = \frac{1}{R} \Rightarrow R = 4 \text{ k}\Omega$$

Taking, $V=0$, we get, $I = \frac{0}{4} + 6 = 6$



So, it goes through $(0, 6) \equiv (0, -I_{sc})$ data point.

$$\therefore 6 = -I_{sc} \Rightarrow I_{sc} = -6 \text{ mA}$$

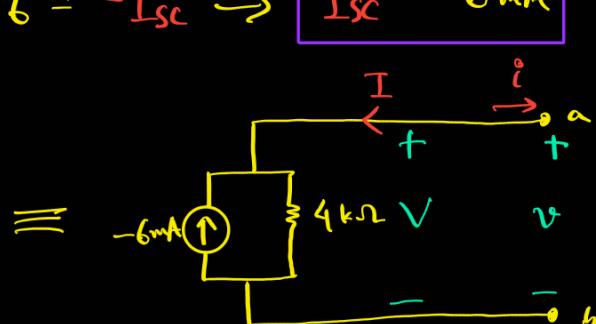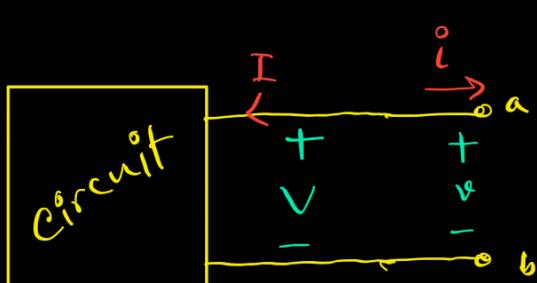

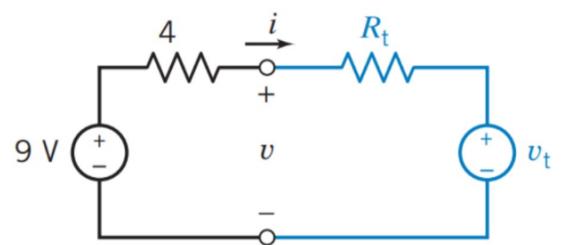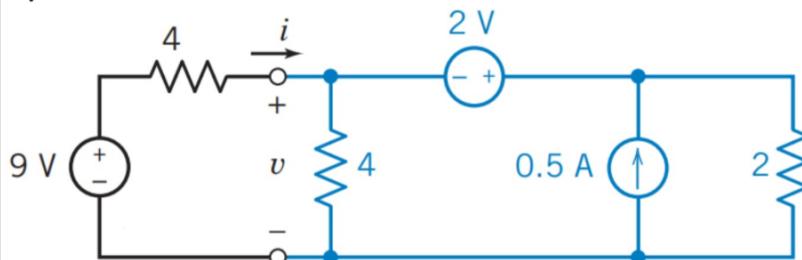
Problem 5

- Determine the values of R_t and v_t , if the following two circuits are equivalent to each other.



Ans: $v_t = -\frac{2}{3}V$, $R_t = \frac{4}{3}\Omega$

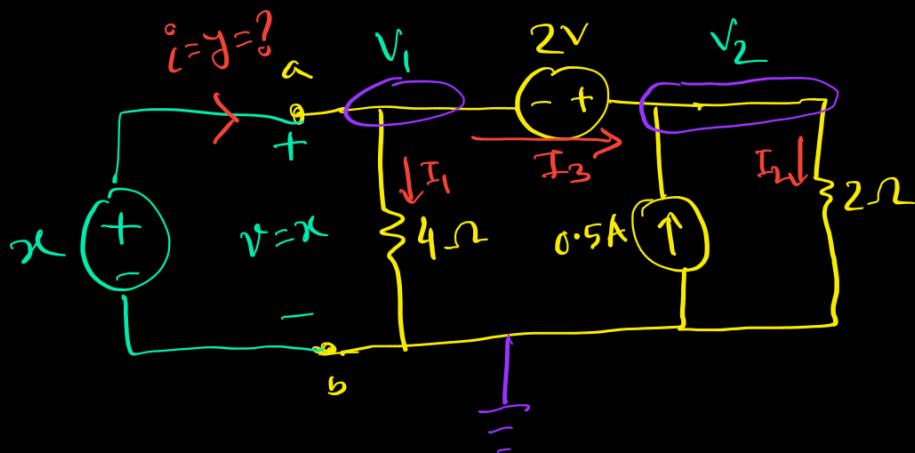Since the black part is same on both circuits, we only need to find the equivalent of the blue part of the circuit.



$$V_1 - 0 = x \Rightarrow V_1 = x$$

$$V_2 - V_1 = 2 \Rightarrow V_2 = V_1 + 2 = x + 2$$

$$I_1 = \frac{V_1 - 0}{4} = \frac{x}{4}, \quad I_2 = \frac{V_2 - 0}{2} = \frac{x+2}{2} = \frac{x}{2} + 1$$

$$\text{KCL @ 2: } -I_3 - 0.5 + I_2 = 0 \Rightarrow I_3 = I_2 - 0.5 = \frac{x}{2} + 1 - 0.5$$

$$\text{KCL @ 1: } x = I_1 + I_3 = \frac{x}{4} + \frac{x}{2} + 1 - 0.5 = \frac{3x}{4} + 0.5$$

$$\text{Solve: } I = \frac{3V}{4} + 0.5$$

Comparing with $y = mx + c$,

$$m = \frac{3}{4} = \frac{1}{R} \Rightarrow R = \frac{4}{3} \Omega$$

In order to find v_t we set $V = v_t$ and $I = 0$,
because the I-V of voltage src + series resistor
gives through $(v_t, 0)$ data point.

$$\text{So, } 0 = \frac{3v_t}{4} + 0.5$$



$$\Rightarrow \frac{3v_t}{4} = -0.5$$

$$\Rightarrow v_t = -0.5 \times \frac{4}{3} = -\frac{2}{3} V$$


$$\therefore \boxed{v_t = -\frac{2}{3} V}$$

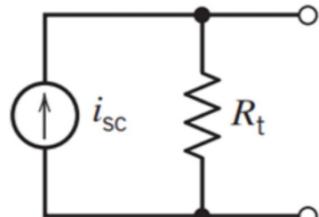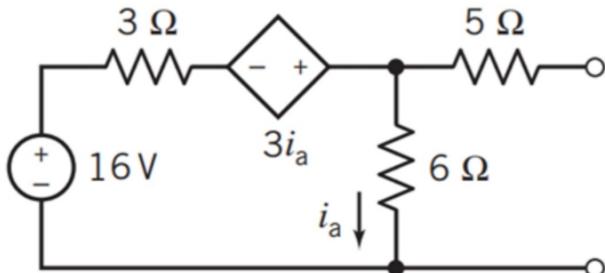Problem 6

- Determine the values of R_t and i_{sc} , if the following two circuits are equivalent to each other.



Ans: $i_{sc} = 2 A$, $R_t = 8 \Omega$

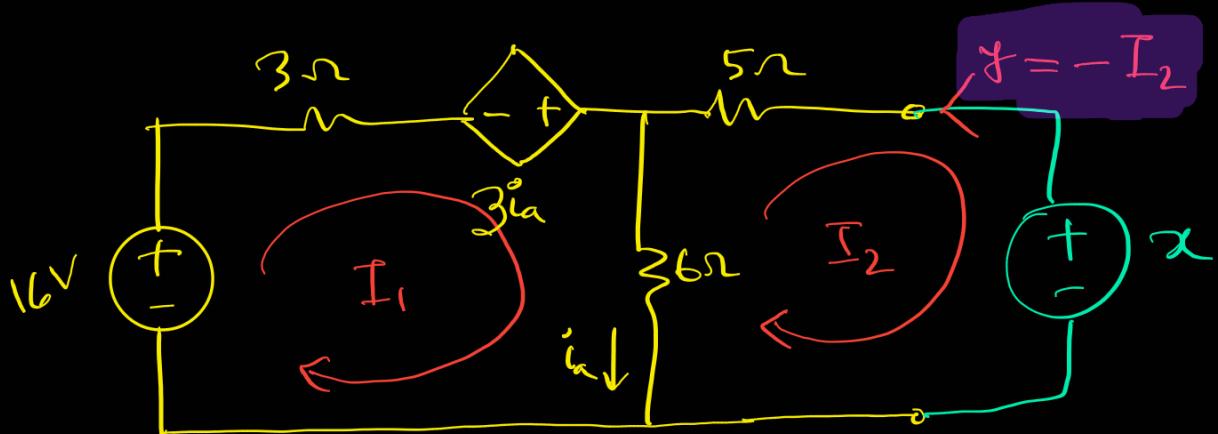

$$\begin{aligned}
 \text{KVL @ 1: } & I_1(3+6) - 6I_2 - 16 - 3i_a = 0 \\
 \Rightarrow & 9I_1 - 6I_2 - 16 - 3(I_1 - I_2) = 0 \\
 \Rightarrow & 6I_1 - 3I_2 - 16 = 0 \\
 \Rightarrow & 6I_1 + 3y - 16 = 0 \quad \text{--- (1)}
 \end{aligned}$$

$$\begin{aligned}
 \text{KVL @ 2: } & I_2(5+6) - 6I_1 + x = 0 \\
 \Rightarrow & 11I_2 - 6I_1 + x = 0 \\
 \Rightarrow & -11y - 6I_1 + x = 0 \quad \text{--- (II)}
 \end{aligned}$$

$$\begin{aligned}
 (1) + (II) \Rightarrow & 6I_1 + 3y - 16 - 11y - 6I_1 + x = 0 \\
 \Rightarrow & 8y = x - 16 \Rightarrow y = \frac{x - 16}{8} \Rightarrow y = \frac{x}{8} - 2
 \end{aligned}$$

Comparing with $y = mx + c$,

$$m = \frac{1}{8} = \frac{1}{R_t} \Rightarrow R_t = 8 \Omega$$

In order to find i_{sc} we set $V=0$ and $I=-i_{sc}$,
because the I-V of current src + parallel resistor
goes through $(0, -i_{sc})$ data point.

$$\text{So, } y = \frac{x}{8} - 2$$



$$\Rightarrow -i_{sc} = \frac{0}{8} - 2$$

$$\Rightarrow -i_{sc}^0 = -2 \text{ A}$$

$$\therefore i_{sc}^0 = 2 \text{ A}$$

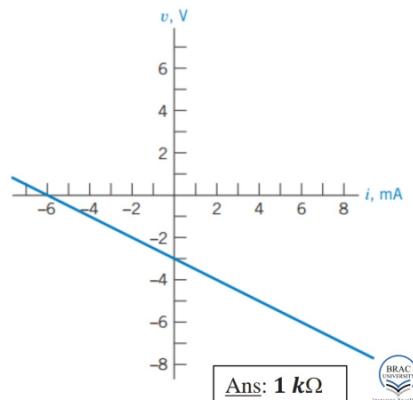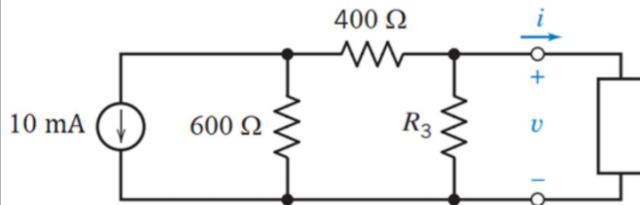Problem 7

- If the voltage v vs. current i has the following relationship expressed graphically, determine the value of R_3 .




Notice that i and v does not follow passive sign convention.

Also notice that the graph axes are flipped.

Here, i is in x-axis and v is in y-axis.

Following passive sign convention:

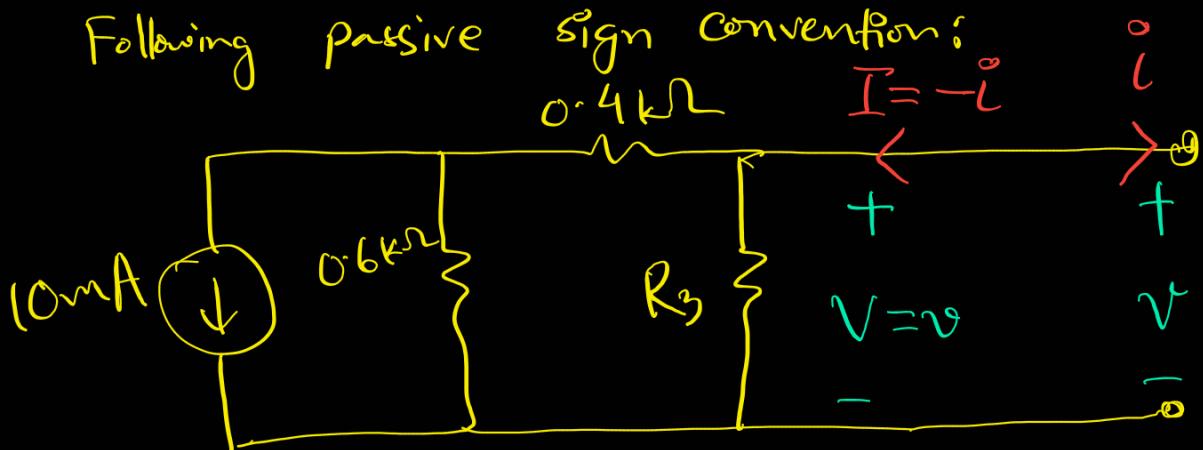

Choosing two data points from graph:

$$\textcircled{1} \quad (-6, 0) \equiv (i_1, v_1) \equiv (-I_1, V_1) \Rightarrow V_1 = 0V, I_1 = 6 \text{ mA}$$


$$\textcircled{2} \quad (0, -3) \equiv (i_2, v_2) \equiv (-I_2, V_2) \Rightarrow V_2 = -3V, I_2 = 0 \text{ mA}$$

$$\therefore m = \frac{V_2 - V_1}{x_2 - x_1} = \frac{I_2 - I_1}{V_2 - V_1} = \frac{0 - 6}{-3 - 0} = 2$$

$$\therefore m = \frac{1}{R} = 2 \Rightarrow R = \frac{1}{2} \text{ k}\Omega = 0.5 \text{ k}\Omega$$

$$\therefore R = 0.5 \text{ k}\Omega$$

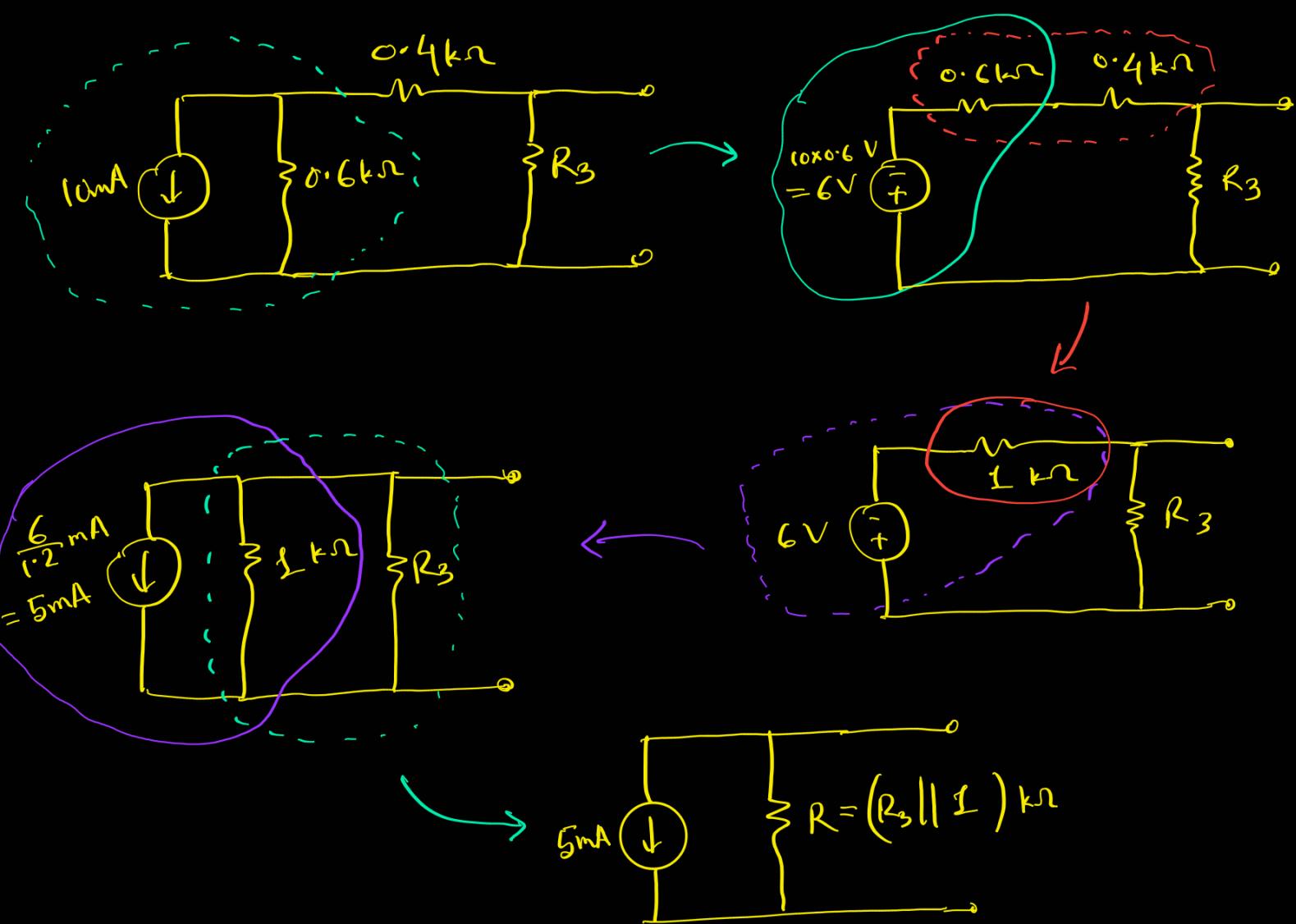This is not R_3 . It is the overall equivalent resistance. We can use source transformation to find the overall equivalent resistance.



Since, R is the parallel equivalent of R_3 and $1 \text{ k}\Omega$,

$$\frac{1}{R} = \frac{1}{R_3} + \frac{1}{1}$$

$$\Rightarrow \frac{1}{0.5} = \frac{1}{R_3} + \frac{1}{1}$$

$$\Rightarrow \frac{1}{R_3} = \frac{1}{0.5} - \frac{1}{1} = 2 - 1 = 1$$

$$\Rightarrow R_3 = 1 \text{ k}\Omega$$